
 


1. Enter the maximum value of the count to run a 5-second timer with a 1 Hz clock.

The maximum value of the counter is 4 (100 in binary), since the frequency of the clock is 1 tick per second (1Hz). We count from 0 to 4 (takes 5 seconds in total).

2. State diagram of the state machine.

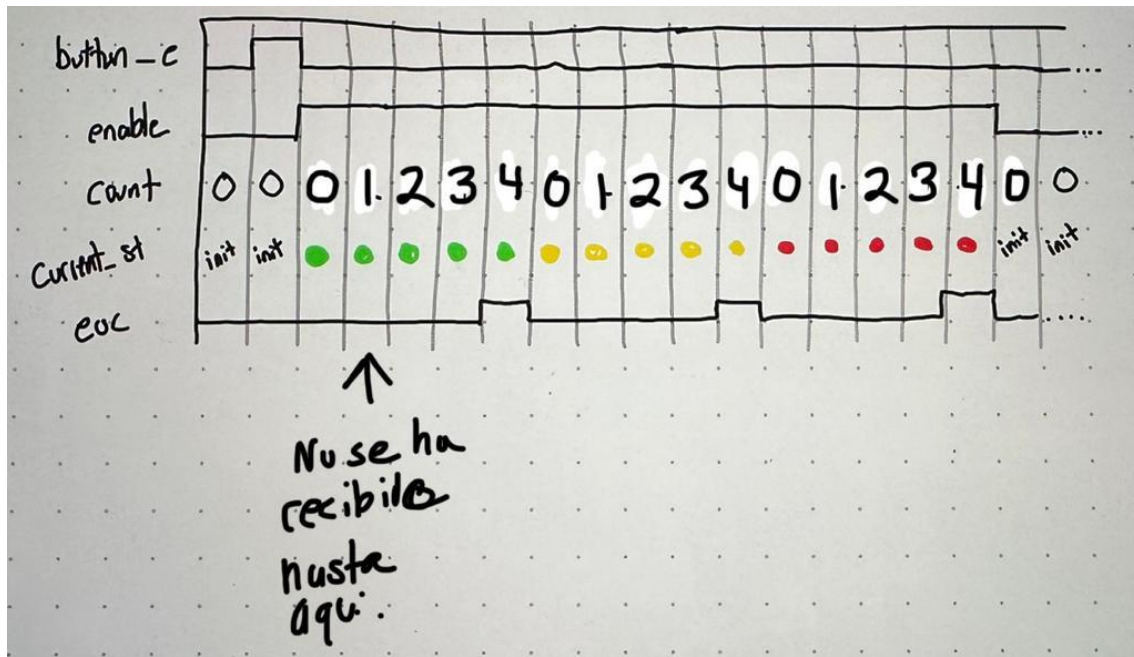



3. VHDL code of the state machine.

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY P1 IS
    PORT (
        button, clk, rst : IN std_logic;
        -- ???, TrainerClock, Switch
        r, y, g : OUT std_logic;
        -- LED2, LED1, LED0
        count_out : OUT std_logic_vector(2 DOWNTO 0)
        -- LED7, LED6, LED5
    );
END P1;

-- NOTE: reset is low active!!! it was a typo
ARCHITECTURE behavior OF P1 IS
    SIGNAL q0 : std_logic;
    SIGNAL q1 : std_logic;
    SIGNAL button_e : std_logic;

    TYPE state IS (initial, green, yellow, red);
    SIGNAL current_st, next_st : state;

    SIGNAL enable : std_logic;
    SIGNAL eoc : std_logic;
    SIGNAL count : unsigned(2 DOWNTO 0);
BEGIN
    count_out <= count(2) & count(1) & count(0);

    -- edge detector

```

```

button_e <= q0 AND (NOT q1);
PROCESS (clk, rst)
BEGIN
    IF (rst = '0') THEN
        q0 <= '0';
        q1 <= '0';
    ELSIF (clk'EVENT AND clk = '1') THEN
        q0 <= button;
        q1 <= q0;
    END IF;
END PROCESS;

-- FSM
PROCESS (current_st, button_e, eoc) BEGIN
    next_st <= current_st; -- default case for when no
action is performed
    CASE current_st IS
        WHEN initial =>
            IF (button_e = '1') THEN
                next_st <= green; -- move to green
state

            END IF;
            r <= '0';
            y <= '0';
            g <= '1';
            enable <= '0';
        WHEN green =>
            IF (eoc = '1') THEN
                next_st <= yellow; -- move to yellow
state

            END IF;
            r <= '0';
            y <= '0';
            g <= '1';
            enable <= '1';
        WHEN yellow =>
            IF (eoc = '1') THEN
                next_st <= red; -- move to red state

            END IF;
            r <= '0';
            y <= '1';
            g <= '0';
            enable <= '1';
        WHEN red =>
            IF (eoc = '1') THEN
                next_st <= initial; -- return to
initial state

            END IF;
            r <= '1';
            y <= '0';
            g <= '0';

```

```

        enable <= '1';
    END CASE;
END PROCESS;

-- triggers state changes each clock signal
PROCESS (clk, rst)
BEGIN
    IF (rst = '0') THEN
        current_st <= initial;
    ELSIF (clk'EVENT AND clk = '1') THEN
        current_st <= next_st;
    END IF;
END PROCESS;

-- timer
-- eoc <= count(2) and not count(1) and not count(0);
eoc <= '1' WHEN count = "100" ELSE '0';
PROCESS (clk, rst)
BEGIN
    IF (rst = '0') THEN
        count <= "000";
    ELSIF (clk'EVENT AND clk = '1') THEN
        IF (enable = '0') THEN
            count <= "000";
        ELSIF (count = "100") THEN
            count <= "000";
        ELSE
            count <= count + 1;
        END IF;
    END IF;
END PROCESS;
END behavior;

```